



# Hardware Technologies for Robust Personal Communication Transceivers

**Henry Samueli**

**Asad A. Abidi**

**Gregory J. Pottie**

**Yahya Rahmat-Samii**

  

**Integrated Circuits & Systems Laboratory  
Electrical Engineering Department  
University of California  
Los Angeles, CA 90024-1594**

# UCLA Low-Power Transceiver Program

**Objective:** Low-power, handheld, robust transceivers for indoor and mobile personal communications


**Means:** Investigate analog, digital, and antenna technologies, coupled tightly to system design

## Robustness


- Space Diversity with Multiple Antennas
- Frequency Diversity with Spread-Spectrum
- Time Diversity with ECC/Interleaving
 
## Low Power Dissipation

- Low-Voltage Custom Analog & Digital CMOS
- Monolithic CMOS 915 MHz Receive/Transmit Path
- Two-chip Design; Minimum Discrete Components


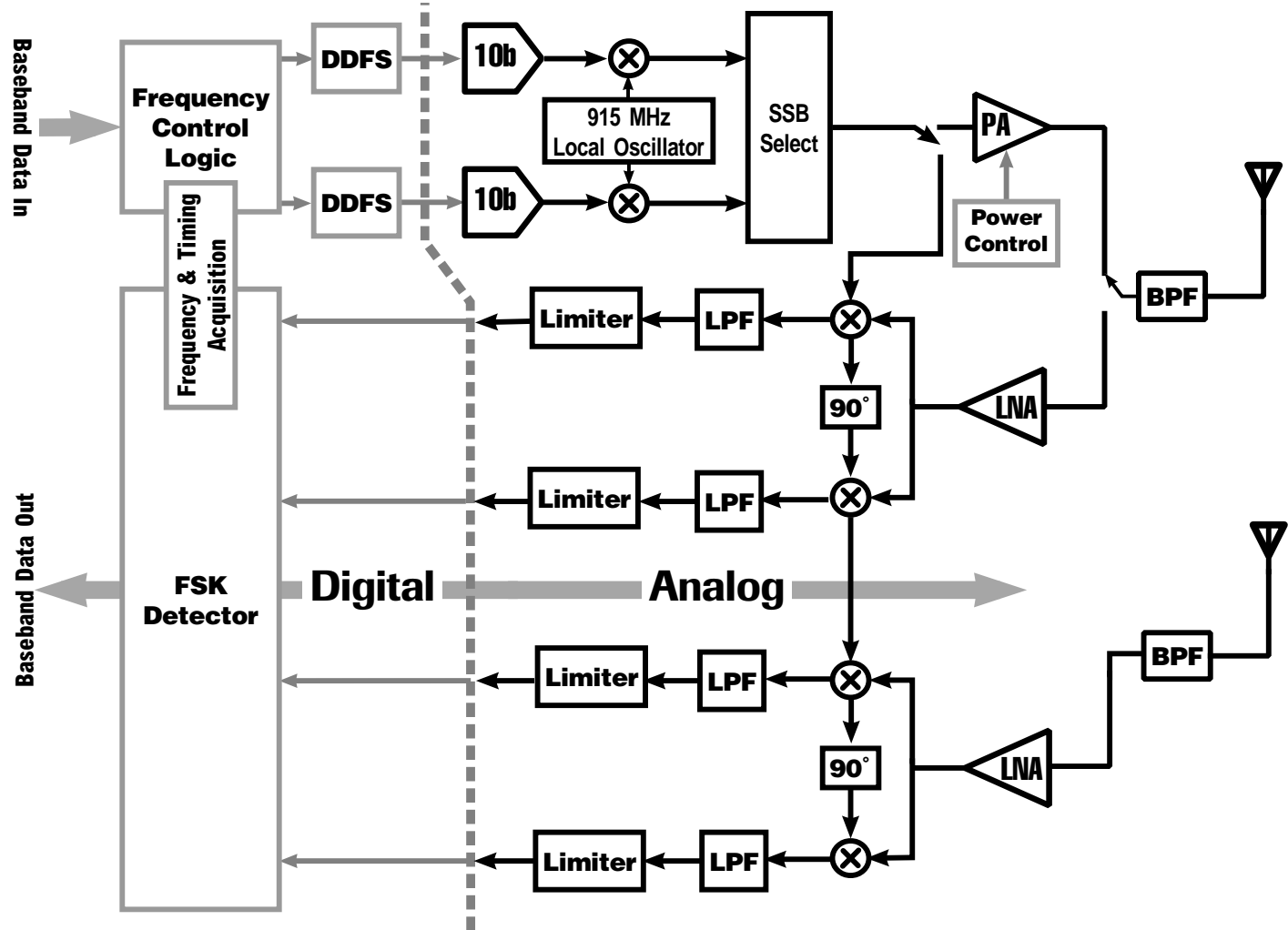
# The UCLA Frequency-Hopped Spread-Spectrum CMOS Transceiver



# Performance Specifications of Handset

<b>Power Dissipation of Handset</b>	225 mW in receive, 300 mW in transmit
<b>Frequency Band</b>	902-928 MHz (unlicensed ISM band)
<b>Radiated Power</b>	20 mW (max); 20 $\mu$ W (min)
<b>Data Rate</b>	2 to 160 kb/s (variable)
<b>Duplexing</b>	Time Division Duplex between TX and RX
<b>Multiple Access Method</b>	Frequency-Hopped Spread-Spectrum CDMA
<b>Coding</b>	Rate- $\frac{1}{2}$ Convolutional Code (k=6)
<b>Modulation</b>	Binary or Quaternary FSK
<b>Power Supply</b>	3 V (max)
<b>IC Technology</b>	1- $\mu$ m bulk CMOS
<b>Receive Antennas</b>	Multiple miniature embedded elements with space and polarization diversity

# Spread-Spectrum Systems: Hardware Implications

## Direct Sequence

- Frequency Diversity by making chip-rate  $\gg$  symbol rate
- Equalization at *chip-rate*  $\Rightarrow$  High-speed signal processing required
- Coherent receiver most common
- Main advantage: SNR gain with coherent detection, optimum modulation
- Limitation: High complexity

## Frequency Hopped

- Covers wide bandwidth with low hop-rate
- Equalization at *hop-rate* only
- Simple binary FSK modulation may be used
- Non-coherent receiver is simple
- Main advantage: Low-power receiver
- Limitation: Sub-optimal channel capacity

# Diversity Techniques

## Multiple Antennas

- Antennas receive uncorrelated signals
- Use space and polarization diversity

## Frequency Spreading




- Code-Division Multiple Access (CDMA); Direct Sequence OR Frequency Hop
- Time-Division Multiple Access (TDMA); Equalization

## Time Diversity

- Coding
- Interleaving


## Power Control

# Power Amplifier

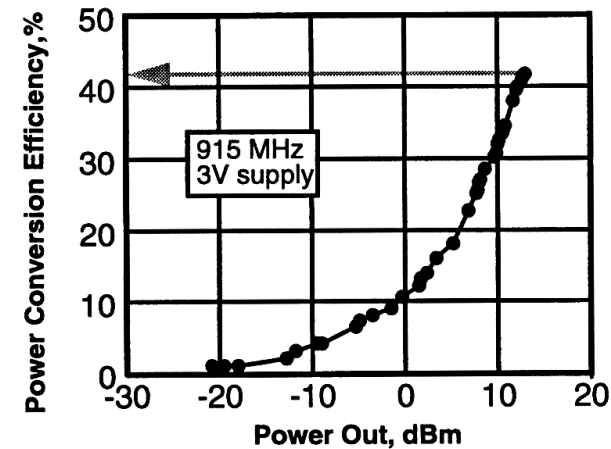 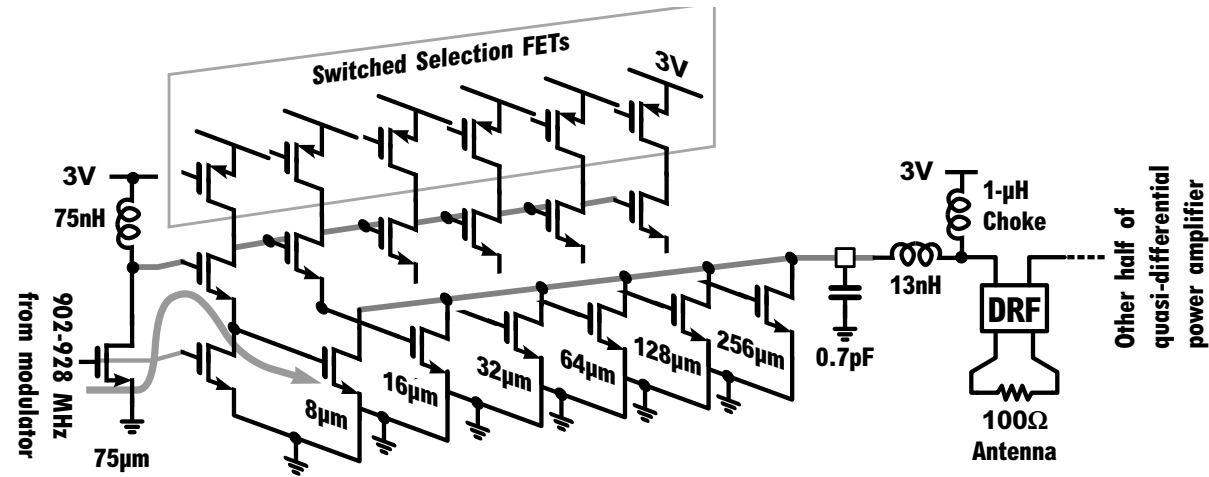

- Amplifier attains 42% power conversion efficiency at +15 dBm output power
- Binary-weighted array of FETs gives 36 dB of power control (6-b word)
- Inductively-loaded preamp drives FETs above 3-V supply
- Off-chip matching network filters out harmonics



# Frequency-Hopped Synthesizer

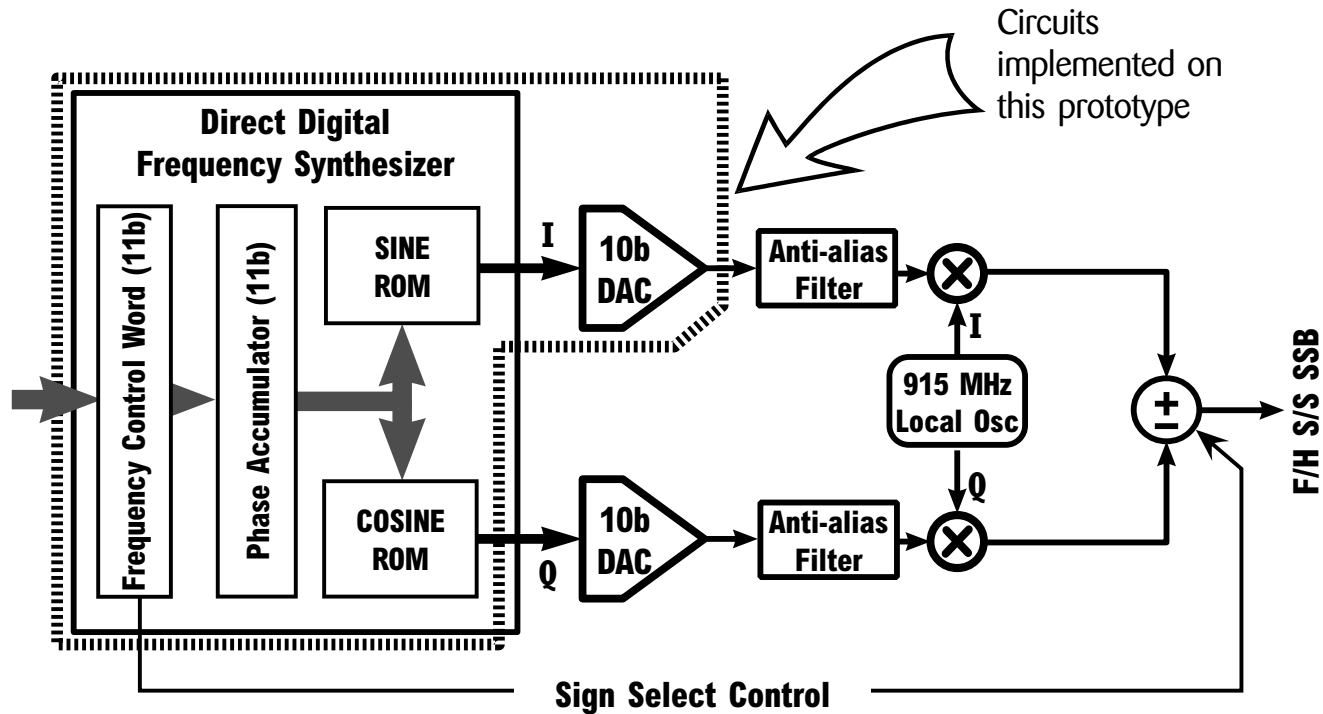

- DDFS produces samples of a sinewave at a frequency selected by 11-b word; instantly agile frequency source
- DDFS output range is 0→13 MHz; *adding* up-converted outputs produces SSB 915→928 MHz; *subtracting* them produces 902→915 MHz
- 8-b matching required between channels for adequate image suppression




# 10-b, 80 MHz D-A Converter

 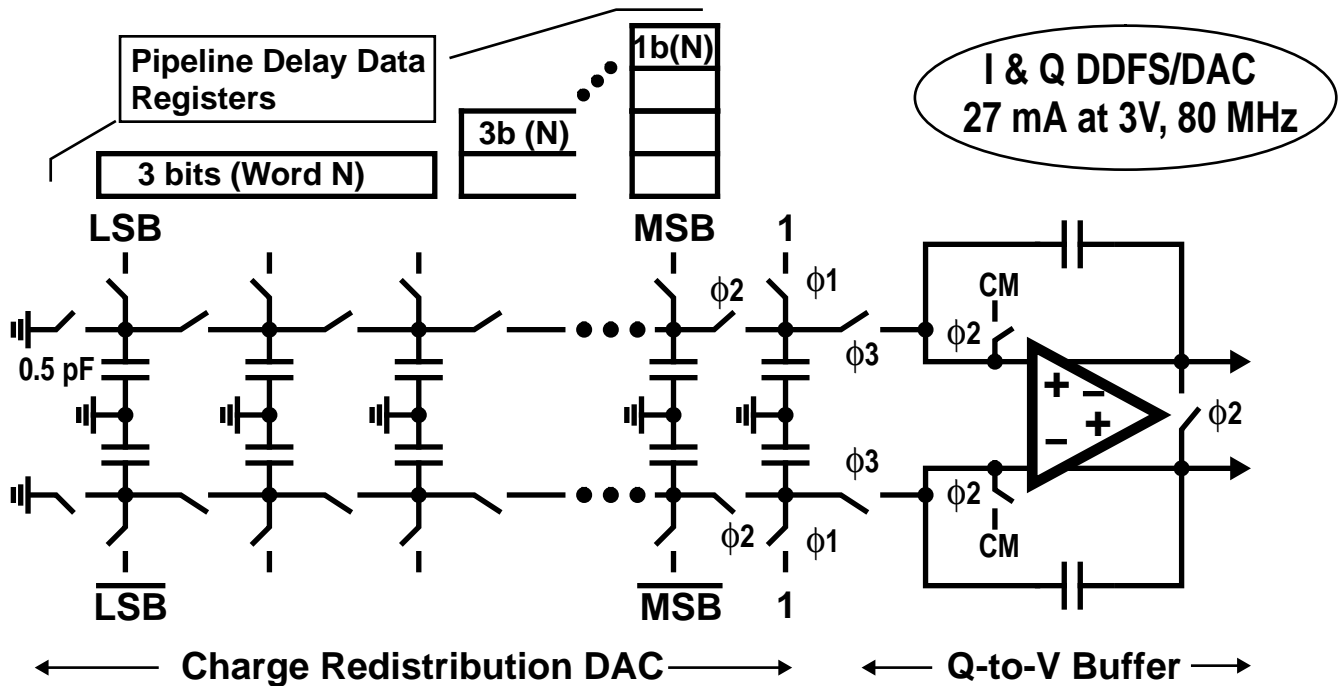


- Low-power through differential implementation using quasi-passive charge-redistribution pipelines
- Linearity limited by capacitance mismatch, voltage-dependent parasitics
- Glitch free!

# Measured DDFS/DAC Spectral Outputs



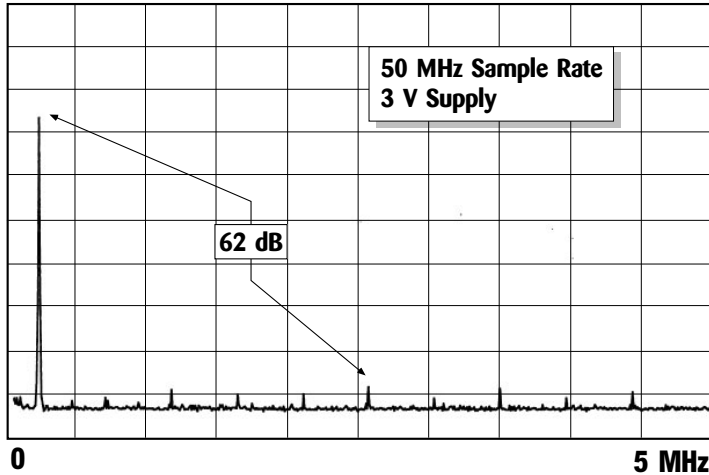


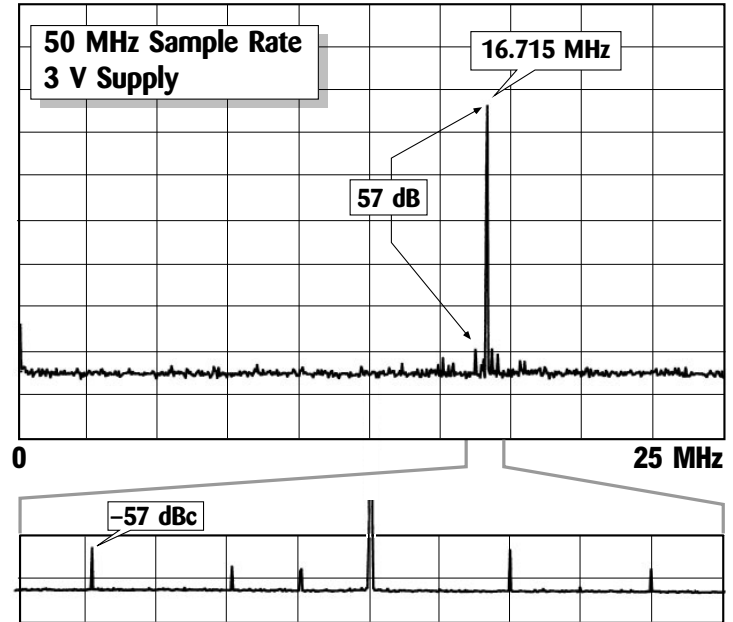- **Spurious level as predicted**
  - set by capacitor mismatch




- **Inter-cell capacitance causes non-linearity at high frequency**




# Baseband Tone-Select Filter

  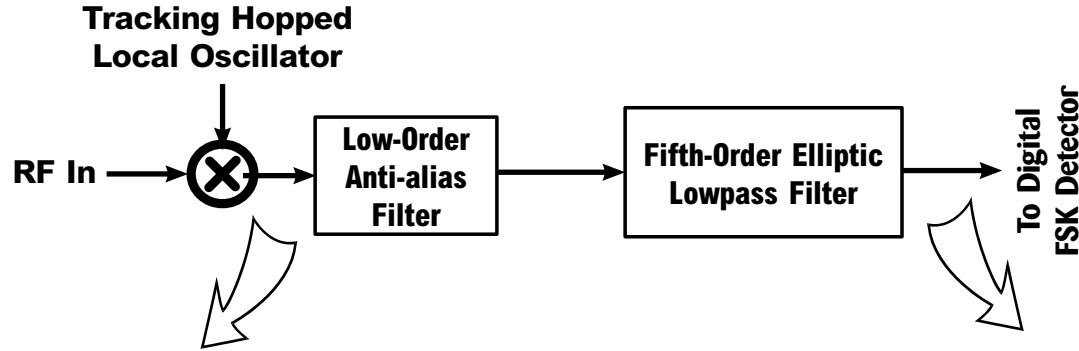




 
- 5th-order Elliptic LPF with 200-kHz cutoff implemented as SCF; dissipates 15 mW from 3-V at 5 MHz sample rate. Operates up to 20 MHz. 60 dB stopband attenuation.
- LPF sets *noise bandwidth* of entire system



# Lowpass Channel-Select Filter

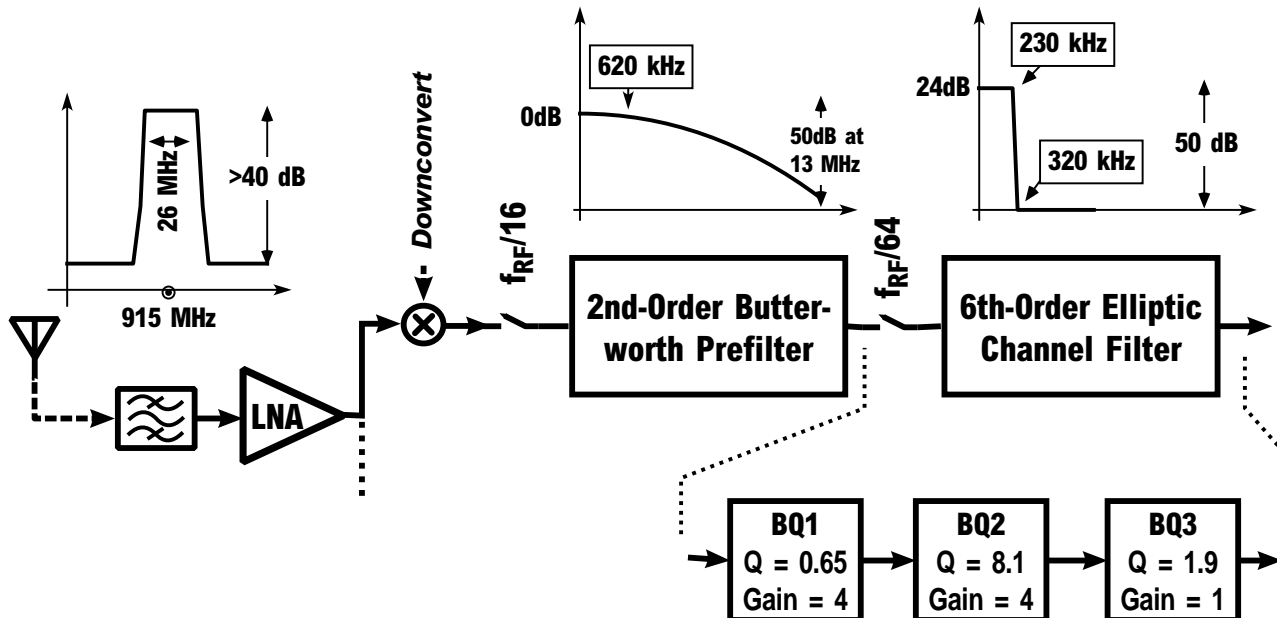  


# Measured Filter Performance

 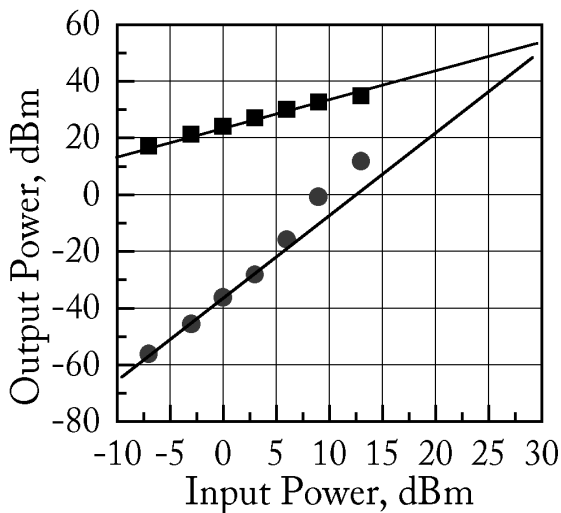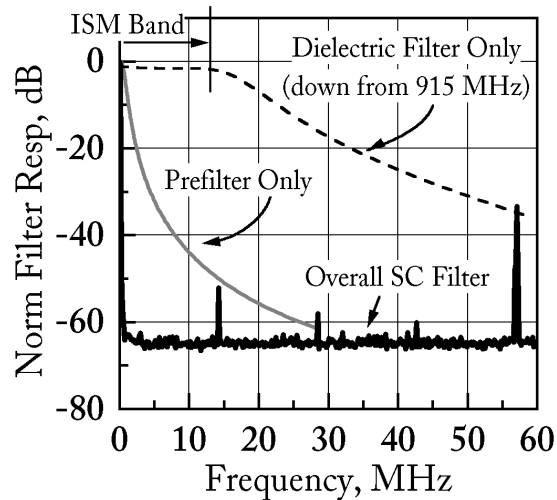 

- 70 nV/Hz in passband
- 4.6 mA from 3V
- 200 pF total on-chip capacitance

# Digital Tone Detector

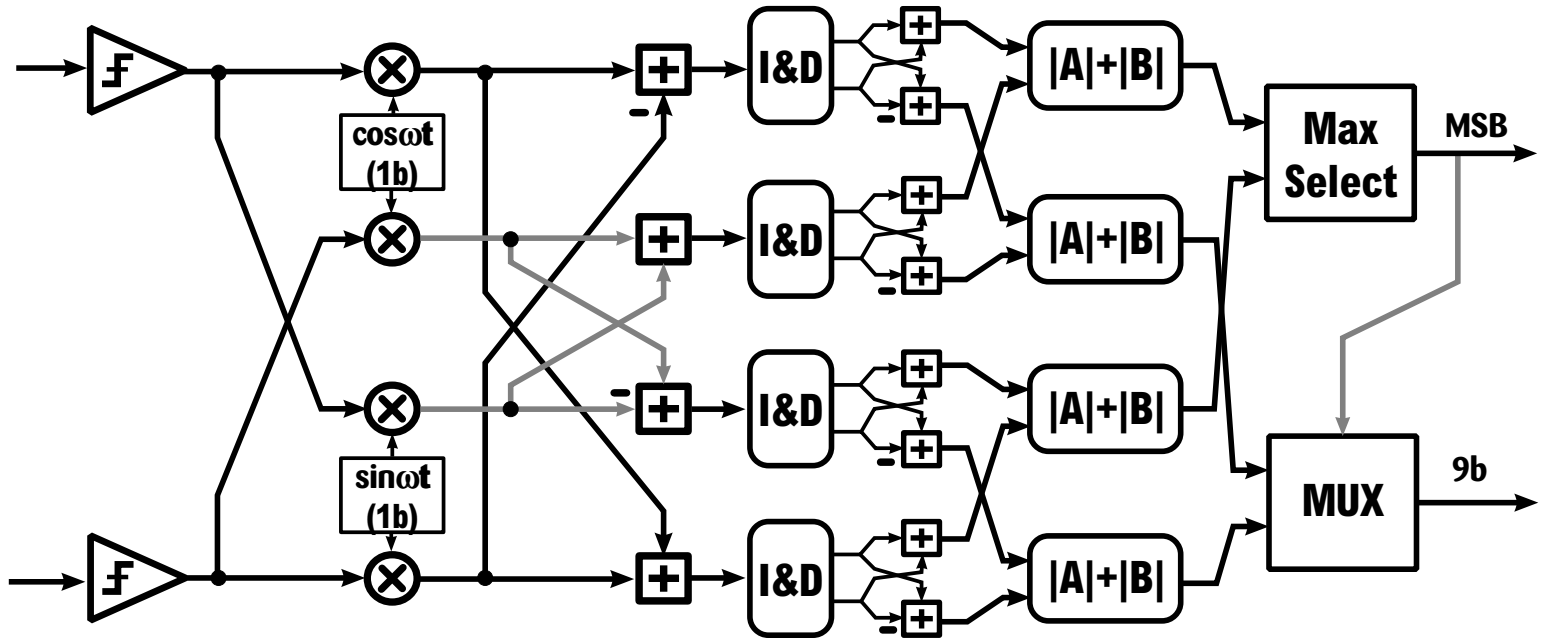

- 1-bit oversampled correlator (programmable oversample rate)
- Multipliers are switches, integrators are accumulators
- 1.9 sq mm active area implementation will dissipate 2 mW

# Rationale Underlying UCLA Low-Power Transceiver

- Radio paging receiver is the most evolved low-energy wireless device today. Receives 500 to 1000 b/s at 400 MHz to 900 MHz.
- Long battery life obtained through very high level of integration (two chips) and optimized system design
- UCLA transceiver uses this as a model. Key extensions are:
  - ✓ *Two-way communication*
  - ✓ *Much higher data rate* ⇨ 160 kb/s (programmable)
  - ✓ *Robust operation in multipath environment* ⇨ *Diversity*
  - ✓ *Large multi-user capacity* ⇨ *CDMA spread-spectrum*


- |   |
|---|
| <p><b>Features</b> ◆ Binary FSK modulation of carrier (like pager)</p> <ul style="list-style-type: none"><li>◆ Frequency-hopped spread-spectrum</li><li>◆ Simple demodulation after de-hopping (like pager)</li><li>◆ Two-chip transceiver (like paging receiver)</li></ul> |
|---|
 
# New Technology for Etching Inductors

Need fast etchant in p+ doped substrates  
Should minimally etch exposed metallization



Xenon DiFluoride ( $\text{XeF}_2$ ) gas-phase etchant



- Etches hemispherical pits anisotropically through array of small holes in oxide
- Depth of etching may be visually monitored through semi-transparent nitride





# 1 GHz Continuous-Time LNA and Mixer

A demonstration of the fundamental capability of MOSFETs to attain *low noise* and *wide dynamic range*, at *low power*

1- $\mu\text{m}$  CMOS operating at 3V; matched to 50 $\Omega$  at input


Drain 8 mA from 3V

  

# LNA Design Rationale

$$\text{Gain} = Q^2 R_s \times g_m = \frac{1}{(\omega_0 C)^2 R_s \times 50\Omega} \approx \left( \frac{50\Omega}{R_s} \right) \left( \frac{\omega_T}{\omega_0} \right)^2$$

Measured  $f_T$  vs  $V_{GS} - V_t$

 


50 nH on-chip inductor load

$R_s \approx 50\Omega$

23 dB gain requires bias at  $(V_{GS} - V_t) = 0.6V$   
for sufficiently high  $f_T$

LNA + mixer drain 8 mA from 3 V

# Channel-Select Filter

 

Current drain of active filter  $\sim 3.5$  mA




Input-referred noise  $\sim 40$  nV/ $\sqrt{\text{Hz}}$

Capacitor spread = 108

Input capacitor  $\sim 0.45$  pF


Output compression point  $\sim 2$  V ptp

# Increasing DDFS/DAC Clock Frequency

  
 


- Eliminate two clock phases,  $\phi_4$  and  $\phi_5$ , in buffer driving on-chip capacitive load
- Rescale DDFS. Carry-select adder in accumulator.
- Use open-loop buffer to drive polyphase filter through four-FET switch upconversion mixers
- 3rd-order distortion, including buffer  $< -45$  dB
 
# Polyphase Filter for Sideband Selection



  
- Extension of the RC-CR phase-shift network, with four-phase inputs and outputs
- Reinforces one sequence of quadrature phases (clockwise, say), while attenuating the other
- Robust against component mismatches (order-of-magnitude better than single-phase network)
- Similarly selects one sideband after upconversion (60 dB rejection with  $10^\circ$  phase error in LO)





# Transmitter Test Chip

6×3.8 mm active area

65 mA active current

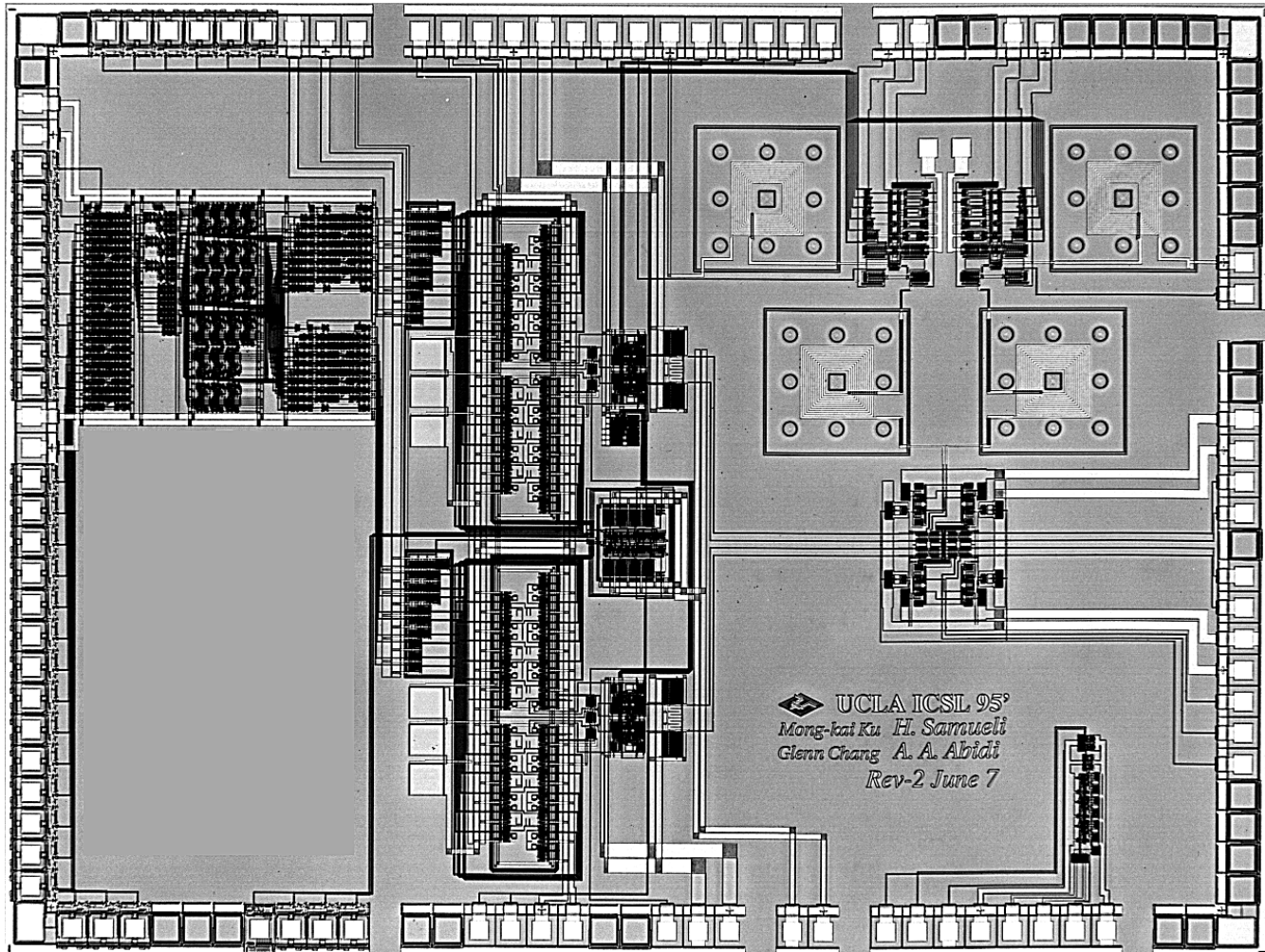


# Transmitter Output Spectra

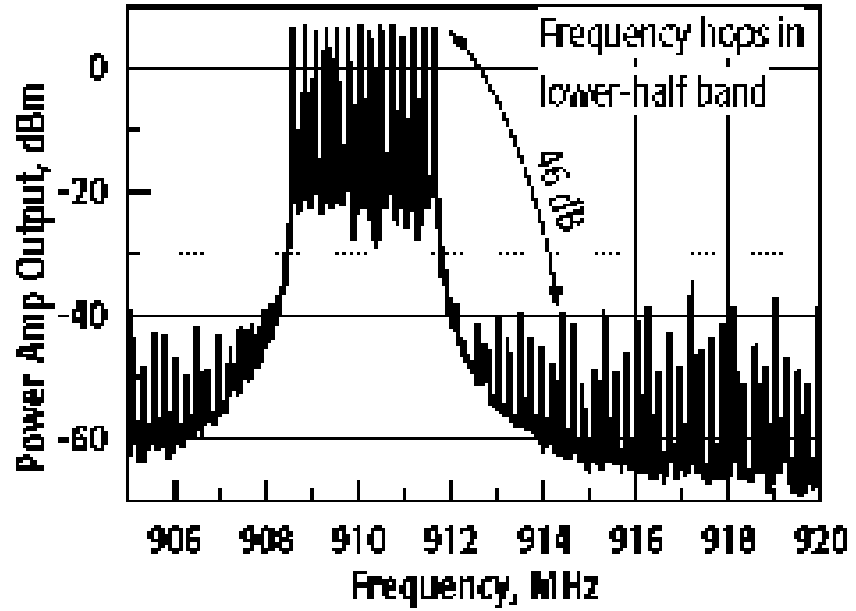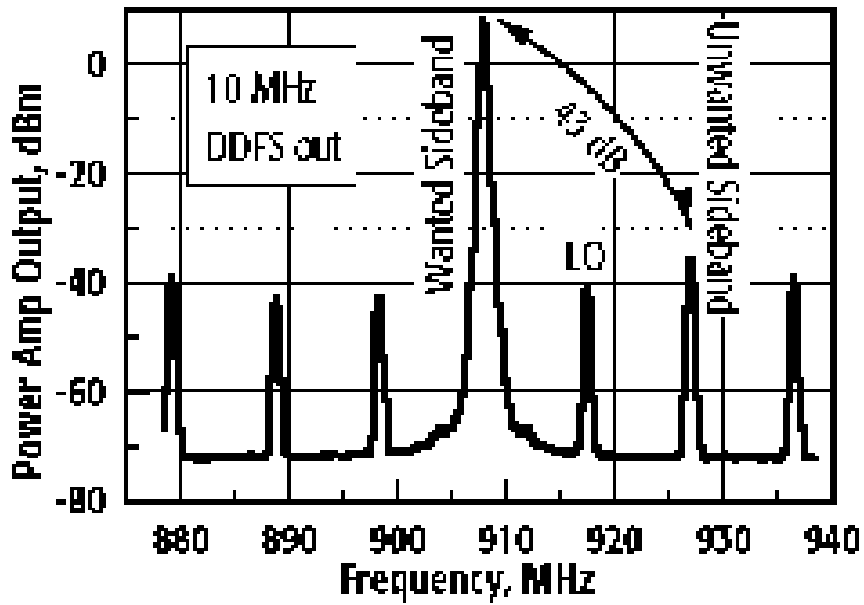

No off-chip filter at power amplifier output  
Measurements at mid-range level +5 dBm

# Current Drain in Transceiver Parts

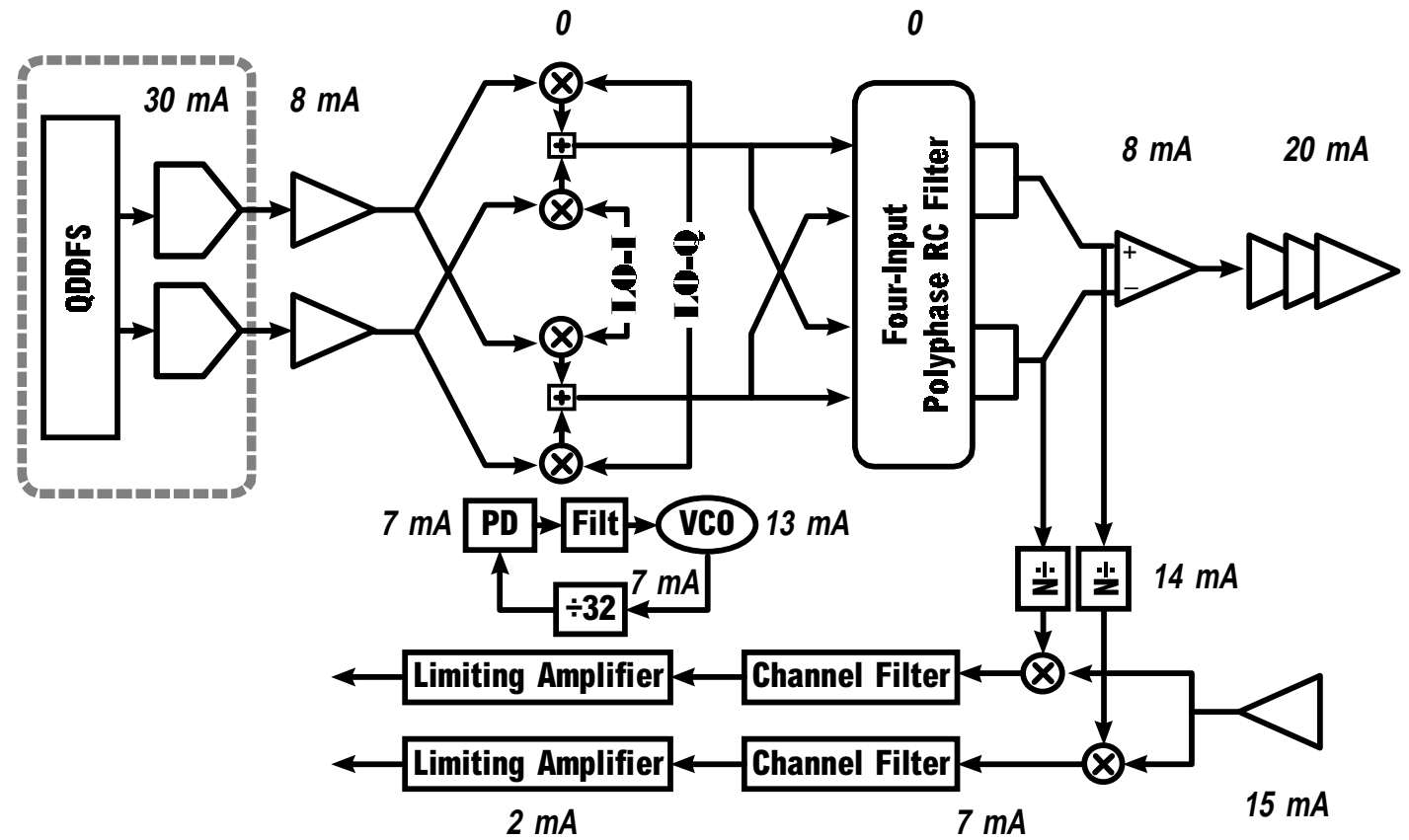



# Measured Performance of Front-End

